


Multiple Choice Questions

Current, Potential Difference, Resistance & Power

Electric Current / Potential Difference / Ohm's Law / Charge Conservation in Circuits / Energy Conservation in Circuits / Resistance in Series & Parallel / Electrical Power / Current-Potential Difference Graphs


Easy (2 questions)	/2
Medium (3 questions)	/3
Total Marks	/5

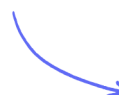Scan here to return to the course
or visit [savemyexams.com](https://www.savemyexams.com)



Easy Questions

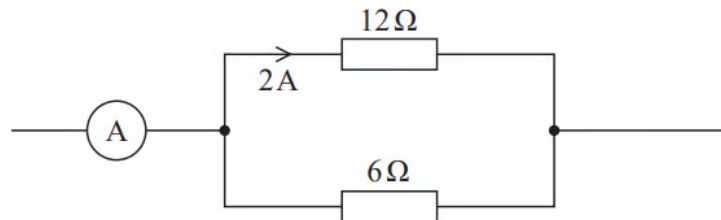- 1 Part of an electric circuit is shown.







What is the current shown by the ammeter?

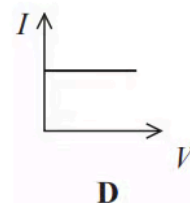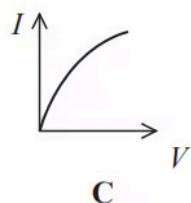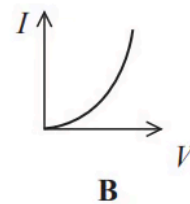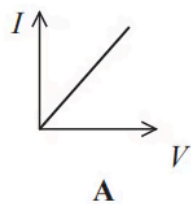- A. 3 A
- B. 4 A
- C. 5 A
- D. 6 A

(1 mark)


- 2 Which of the following graphs shows how the current varies with potential difference for a filament lamp?



(1 mark)

Medium Questions

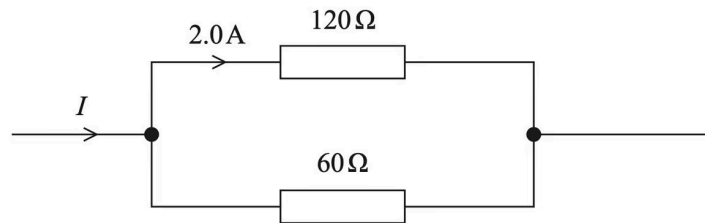- 1 Two resistors are connected in parallel and the current in one of them is 2.0 A, as shown.




Which of the following is the current I in ampere?

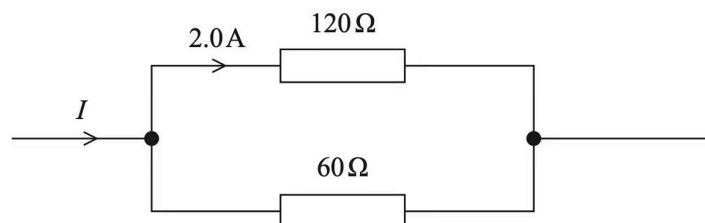- A. 3.0
- B. 4.0
- C. 5.0
- D. 6.0

(1 mark)


- 2 Which of the following is the total resistance of the resistors in parallel?



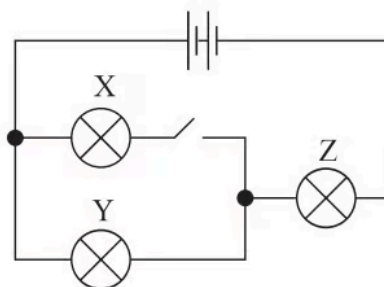- A. $20\ \Omega$
- B. $40\ \Omega$
- C. $90\ \Omega$
- D. $180\ \Omega$

(1 mark)

3 A circuit consists of three identical 1.5 V bulbs connected to two 1.5 V cells.



The switch is closed. Which row describes the change in brightness of bulb Y and bulb Z?

	Y	Z
A	brighter	brighter
B	brighter	dimmer
C	dimmer	brighter
D	dimmer	dimmer

(1 mark)