


Multiple Choice Questions

E.M.F & Modelling Resistance

Electromotive Force / Internal Resistance / E.M.F. vs. Terminal Potential Difference
/ Core Practical 3: Investigating E.M.F. & Internal Resistance / Resistance &
Temperature / Resistance & Illumination


Easy (1 question)	/1
Medium (2 questions)	/2
Total Marks	/3

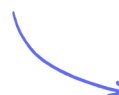Scan here to return to the course
or visit [savemyexams.com](https://www.savemyexams.com)



Easy Questions

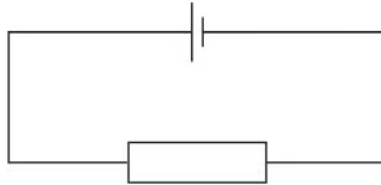- 1 A cell of e.m.f. 1.5 V is connected to a $5.0\ \Omega$ resistor. The terminal potential difference across the cell is 1.0 V .



Which of the following is the current in the circuit?

- A.** 0.1 A
- B.** 0.2 A
- C.** 0.3 A
- D.** 0.5 A

(1 mark)

Medium Questions


- 1 A cell is connected across a resistor. After a while the internal resistance of the cell increases.

Which row of the table correctly shows the change in the current in the circuit and the change in the terminal potential difference across the cell?

	Current	Terminal potential difference
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases

(1 mark)

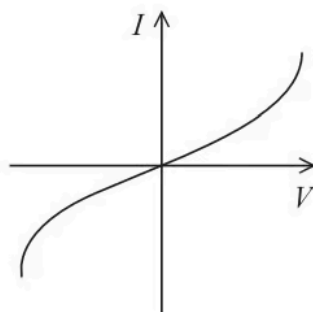- 2 The diagram shows a graph of current I against potential difference V for an electrical component.



Which of the following components would produce a graph of this shape?

- A.** filament bulb
- B.** metallic conductor
- C.** negative temperature coefficient thermistor
- D.** ohmic conductor

(1 mark)